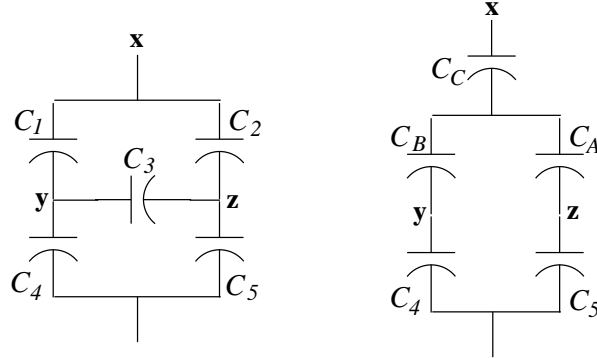


Extra Credit – Equivalent Capacitance
PHYS 1444-001
 Robert Ramsey
 David Joseph Stith



Consider the following:

$$C_A = \frac{C_1 C_2 + C_2 C_3 + C_1 C_3}{C_1}$$

$$C_B = \frac{C_1 C_2 + C_2 C_3 + C_1 C_3}{C_2}$$

$$C_C = \frac{C_1 C_2 + C_2 C_3 + C_1 C_3}{C_3}$$

We first show that the C_1, C_2, C_3 ‘delta’ complex is equivalent to the C_A, C_B, C_C ‘Y’ complex by showing that each of C_{xy}, C_{xz}, C_{yz} in one complex is equivalent to the corresponding pair in the other. In the ‘delta’ circuit, we have:

$$C_{xy} = C_1 + \frac{1}{\frac{1}{C_2} + \frac{1}{C_3}} = C_1 + \frac{C_2 C_3}{C_2 + C_3} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_2 + C_3}$$

$$C_{xz} = C_2 + \frac{1}{\frac{1}{C_1} + \frac{1}{C_3}} = C_2 + \frac{C_1 C_3}{C_1 + C_3} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_1 + C_3}$$

$$C_{yz} = C_3 + \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = C_3 + \frac{C_1 C_2}{C_1 + C_2} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_1 + C_2}$$

and in the ‘Y’ circuit, we have:

$$C_{xy} = \frac{1}{\frac{1}{C_B} + \frac{1}{C_C}} = \frac{1}{\frac{C_2 + C_3}{C_1 C_2 + C_1 C_3 + C_2 C_3}} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_2 + C_3}$$

$$C_{xz} = \frac{1}{\frac{1}{C_A} + \frac{1}{C_C}} = \frac{1}{\frac{C_1 + C_3}{C_1 C_2 + C_1 C_3 + C_2 C_3}} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_1 + C_3}$$

$$C_{yz} = \frac{1}{\frac{1}{C_A} + \frac{1}{C_B}} = \frac{1}{\frac{C_1 + C_2}{C_1 C_2 + C_1 C_3 + C_2 C_3}} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_1 + C_2}$$

These are clearly equal to the ‘delta’, therefore the two circuits are equivalent.

Now we can find an equivalent capacitor for the entire circuit on the right using the simpler series and parallel relationships. This will then also represent an equivalent capacitor for the circuit on the left since the two circuits are equivalent.

Let $Z = C_1C_2 + C_1C_3 + C_2C_3$. Then:

$$\begin{aligned}
C_{eq} &= \frac{1}{\frac{1}{C_C} + \frac{1}{\frac{1}{\frac{1}{C_B} + \frac{1}{C_4}} + \frac{1}{\frac{1}{C_A} + \frac{1}{C_5}}}} \\
&= \frac{1}{\frac{C_3}{Z} + \frac{1}{\frac{C_2}{Z} + \frac{1}{C_4} + \frac{C_1}{Z} + \frac{1}{C_5}}} \\
&= \frac{1}{\frac{C_3}{Z} + \frac{1}{\frac{C_4Z}{Z+C_2C_4} + \frac{C_5Z}{Z+C_1C_5}}} \\
&= \frac{1}{\frac{C_3}{Z} + \frac{1}{\frac{C_4Z(Z+C_1C_5) + C_5Z(Z+C_2C_4)}{(Z+C_2C_4)(Z+C_1C_5)}}}} \\
&= \frac{1}{\frac{C_3}{Z} + \frac{(Z+C_2C_4)(Z+C_1C_5)}{Z(C_4Z+C_1C_4C_5+C_5Z+C_2C_4C_5)}}} \\
&= \frac{1}{\frac{C_3C_4Z + C_1C_3C_4C_5 + C_3C_5Z + C_2C_3C_4C_5 + (Z+C_2C_4)(Z+C_1C_5)}{Z(C_4Z+C_1C_4C_5+C_5Z+C_2C_4C_5)}}} \\
&= \frac{Z(C_4Z + C_1C_4C_5 + C_5Z + C_2C_4C_5)}{Z(C_3C_4 + C_3C_5 + Z + C_1C_5 + C_2C_4) + C_1C_3C_4C_5 + C_2C_3C_4C_5 + C_1C_2C_4C_5} \\
&= \frac{Z(C_4Z + C_5Z + C_1C_4C_5 + C_2C_4C_5)}{Z(C_3C_4 + C_3C_5 + Z + C_1C_5 + C_2C_4) + C_4C_5Z} \\
&= \frac{Z(C_4 + C_5) + C_1C_4C_5 + C_2C_4C_5}{C_3C_4 + C_3C_5 + Z + C_1C_5 + C_2C_4 + C_4C_5} \\
&= \frac{C_1C_2C_4 + C_1C_3C_4 + C_2C_3C_4 + C_1C_2C_5 + C_1C_3C_5 + C_2C_3C_5 + C_1C_4C_5 + C_2C_4C_5}{C_3C_4 + C_3C_5 + C_1C_2 + C_1C_3 + C_2C_3 + C_1C_5 + C_2C_4 + C_4C_5}
\end{aligned}$$

Rearranging the terms in order of subscripts, we state the equivalent capacitance:

$$C_{eq} = \frac{C_1C_2C_4 + C_1C_2C_5 + C_1C_3C_4 + C_1C_3C_5 + C_1C_4C_5 + C_2C_3C_4 + C_2C_3C_5 + C_2C_4C_5}{C_1C_2 + C_1C_3 + C_1C_5 + C_2C_3 + C_2C_4 + C_3C_4 + C_3C_5 + C_4C_5}$$